



DESIGN EVOLUTION OF ANTENNA SYSTEMS FOR DTV MULTICHANNEL OPERATION

- 1.- An Improved Constant Impedance Channel Combiner for UHF TV (MCI)
- 2.- UHF CPOL/EPOL Panel antenna to ensure mobile-handheld reception (RYMSA)

An Improved Constant Impedance Channel Combiner for UHF TV

Presented by Frank Malanga

Micro Communications, Inc.
Merrimack, New Hampshire
A RYMSA Company



Agenda

- Review
 - Different types of channel combiners.
 - Constant-impedance channel combiner (CICC) fundamentals.
- Tutorial
 - The critical role of the hybrid in a CICC.
- New
 - Improved performance of a new 90° coax hybrid designed for wideband, high power channel combining.
 - An Improved Constant Impedance Channel Combiner for UHF TV

Various Types of Channel Combiners


Tee-based Combiners

- Starpoint
- Manifold

Hybrid-based Combiners

- Constant Impedance


Tee-based Combiners

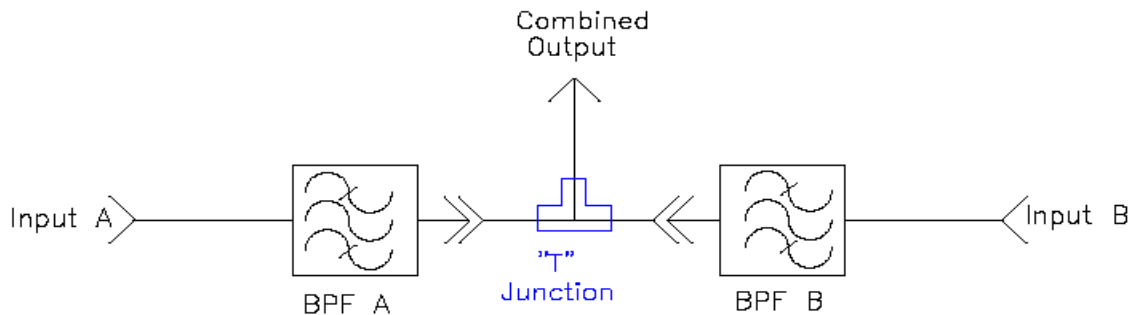

Unitary Tee-junction Combiner


- Starpoint and manifold channel combiners are both composed of the unitary Tee-junction combiners.

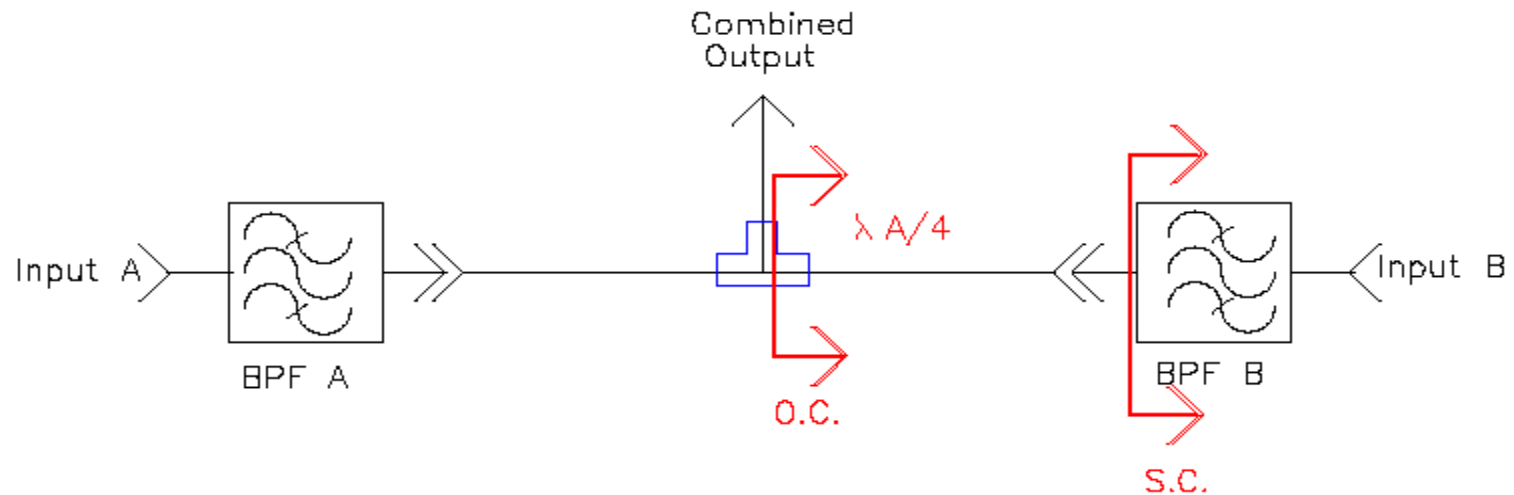Unitary Tee-junction Combiner Channel A Perspective




- BPF-B acts as a short-circuit to Channel A
- One-quarter wavelength before a short circuit is a virtual open circuit
- This open circuit condition effectively decouples the entire “B” branch of the circuit from the tee junction.

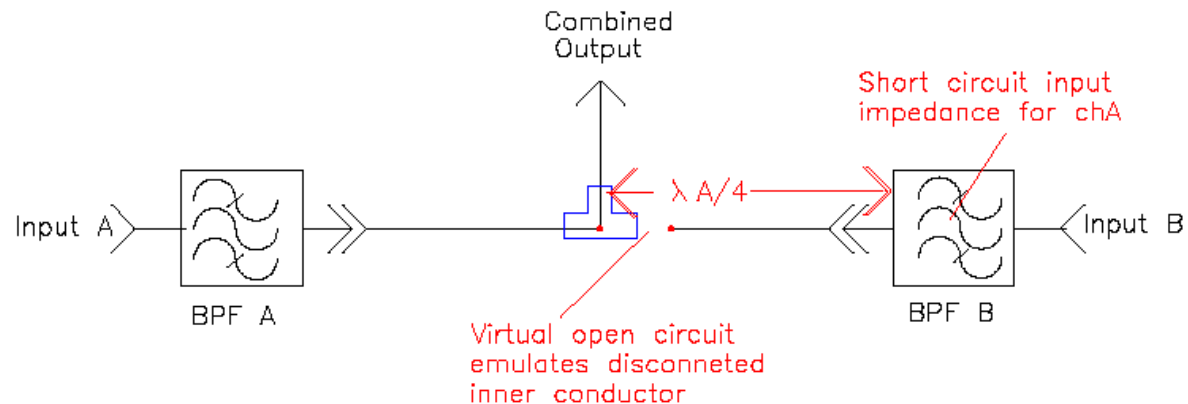Tee-junction Combiner (Channel A perspective)




- A virtual open circuit condition (no current flow) precisely located at the tee junction is effectively similar to disconnecting the inner conductor that leads to filter BPF-B.
- Thus the tee junction with a properly phased reflective filter behaves like an elbow and all power flows to the common output port.

T-junction Combiner General Solution

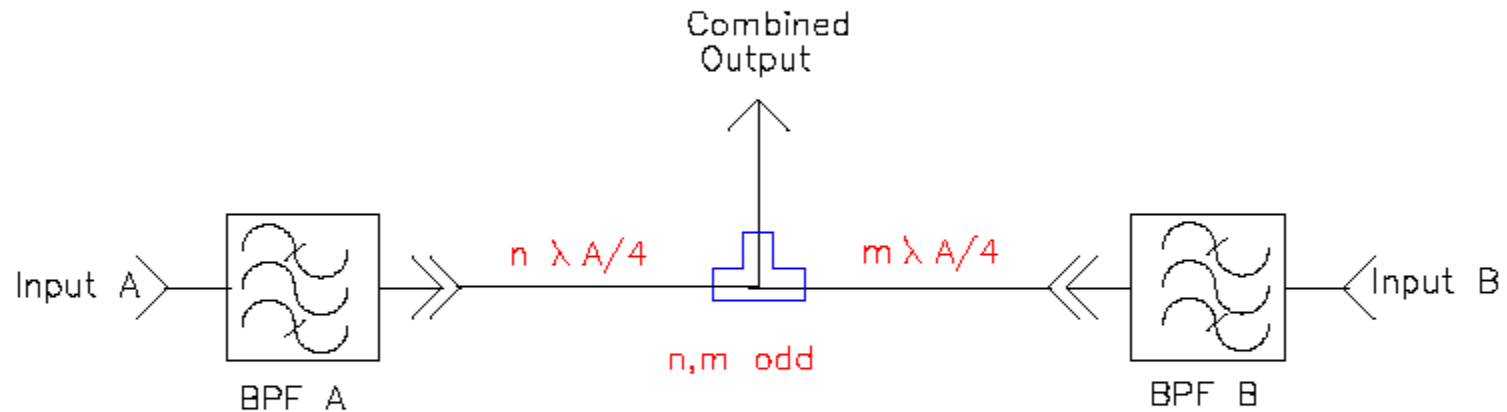


- The line length from BPF-A to the tee junction is critical to channel B and of no consequence to channel A.
- The line length from BPF-B to the tee junction is critical to channel A and of no consequence to channel B.
- Half wavelengths can be added to the phasing lines and the combiner will still work, but with reduced bandwidth. (The critical phasing lines are $\lambda/4$ long at only one center frequency).

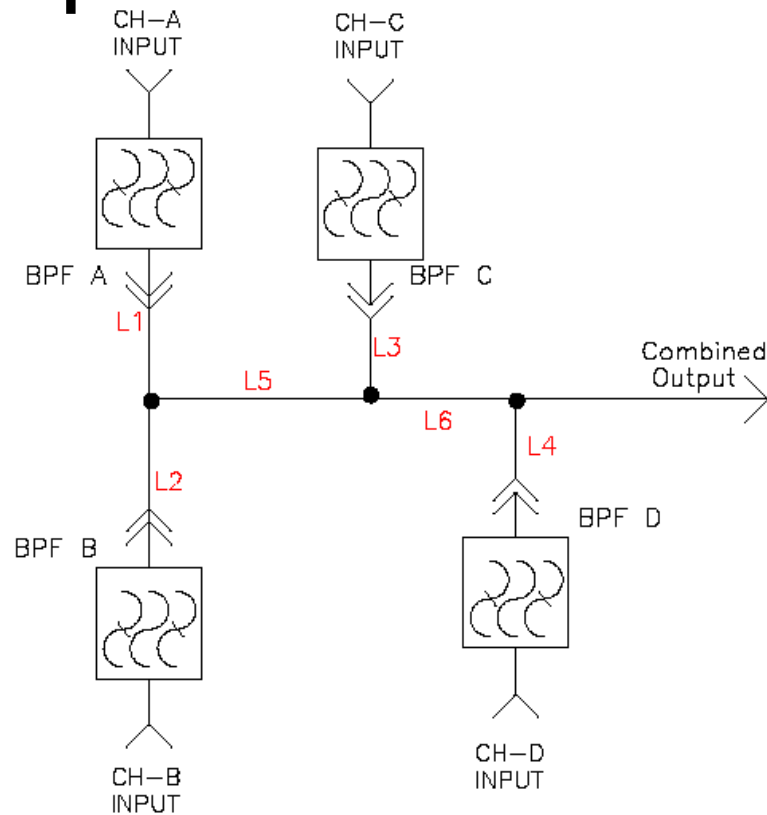Multichannel Tee-junction “Starpoint” Combiners



- Multiple channels can be combined in the same way using multiple tees and multiple phasing lines.

Manifold Combiners

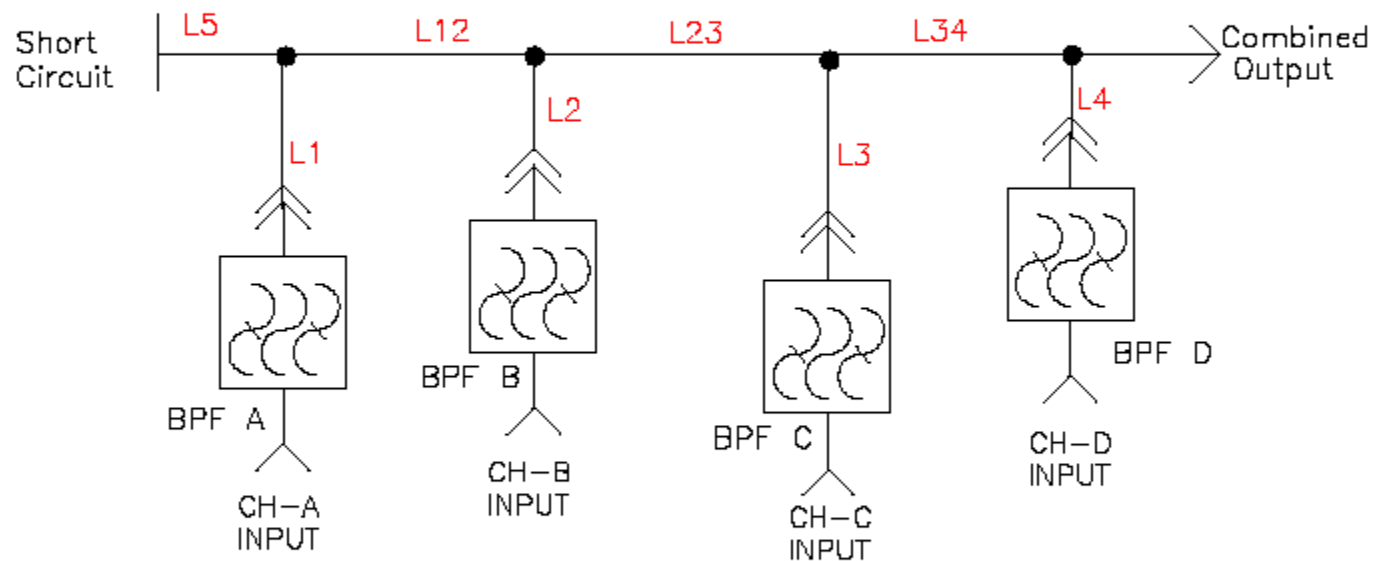


- A manifold combiner is simply a multi-channel tee-combiner with all of the tees lined up in a serial, collinear fashion.


Manifold/Starpoint Combiners

- Can be very compact, with the least hardware for any type of channel combiner.
- Typically lower cost than constant impedance channel combiners.
- Will reflect out-of-band power back to each transmitter.
- Lowest VSWR for any type of channel combiner for multiple widely-spaced channels. (No hybrid)
- Complicated design, very hard to tune the prototype if it is not accurately designed.
- Not future-expandable. (But it can be fed into the wideband input port of a downstream constant-impedance channel combiner.)

Four-Channel Starpoint Combiner

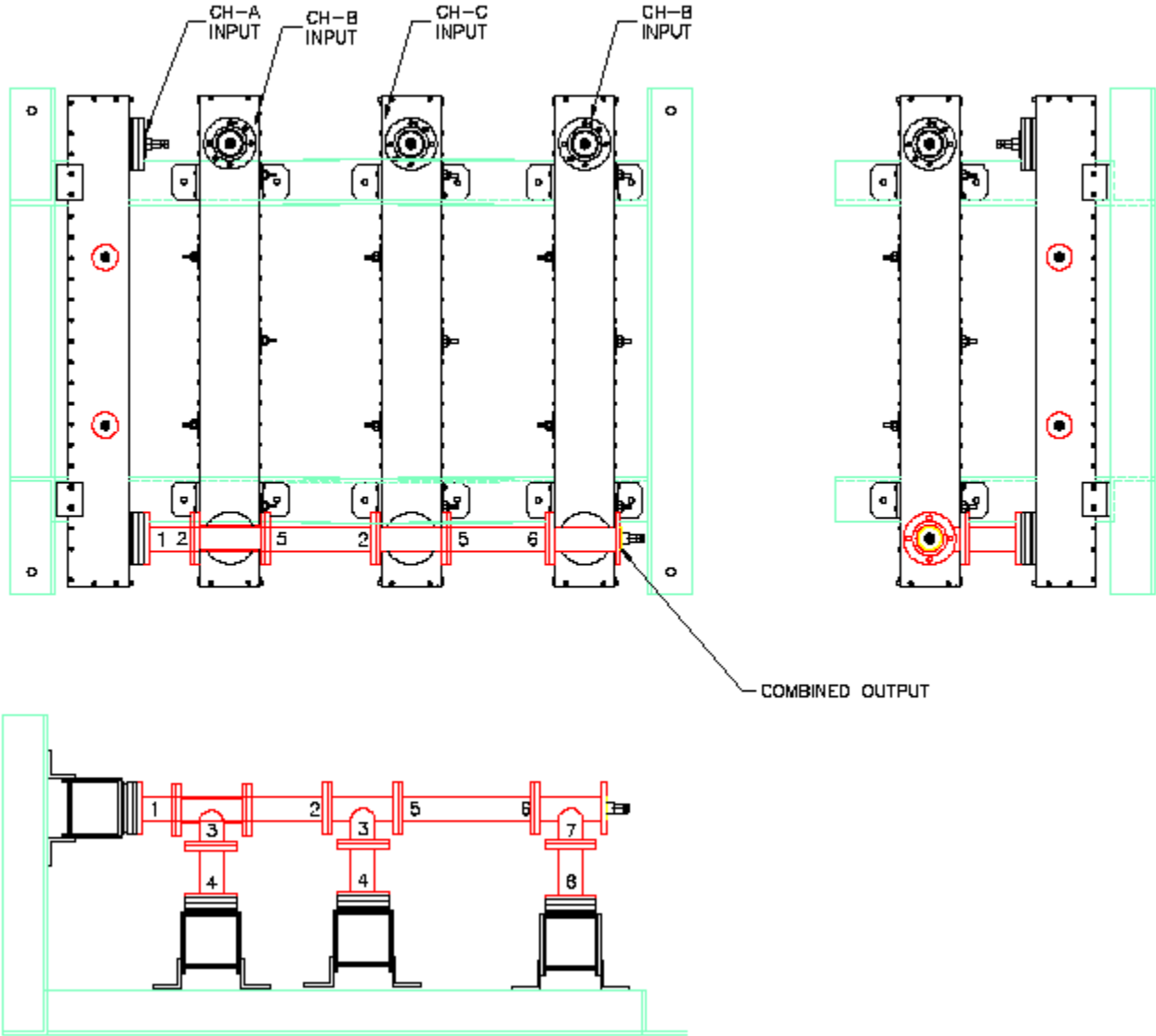


Five-channel Manifold Combiner

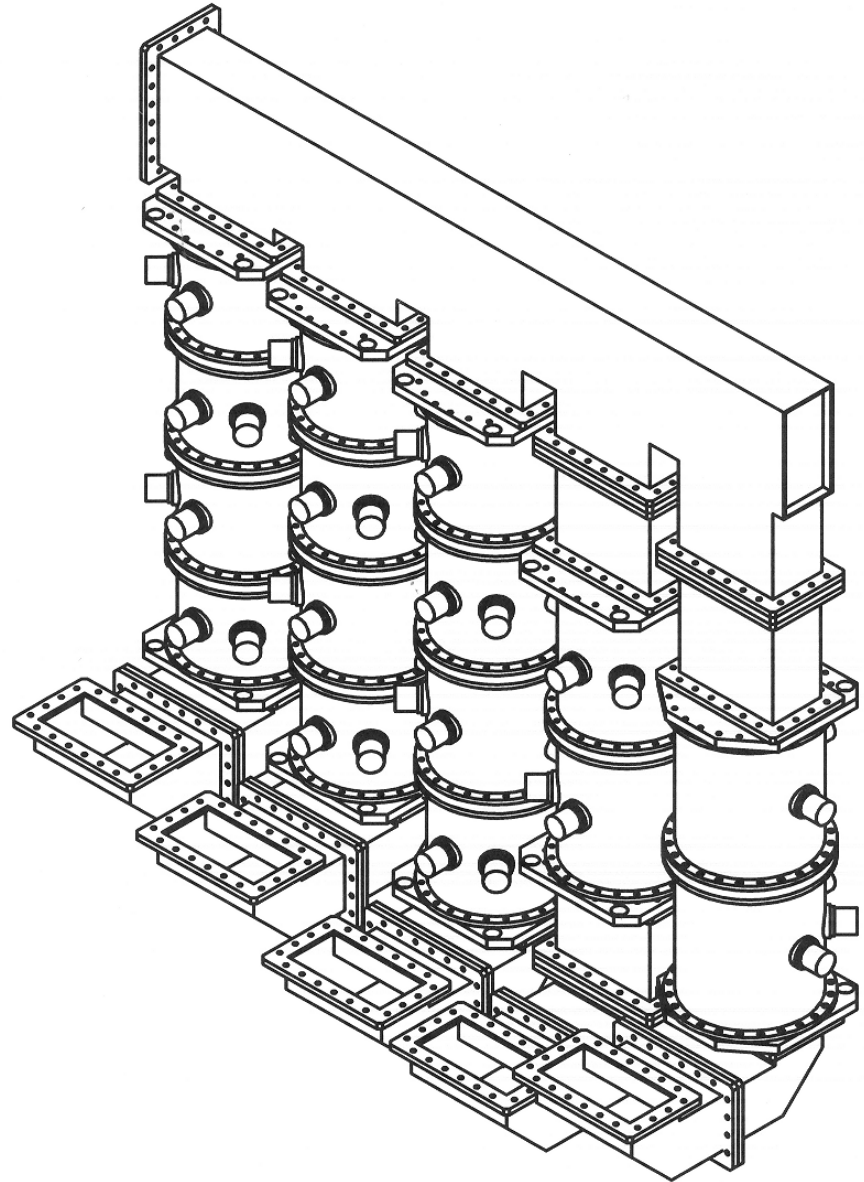




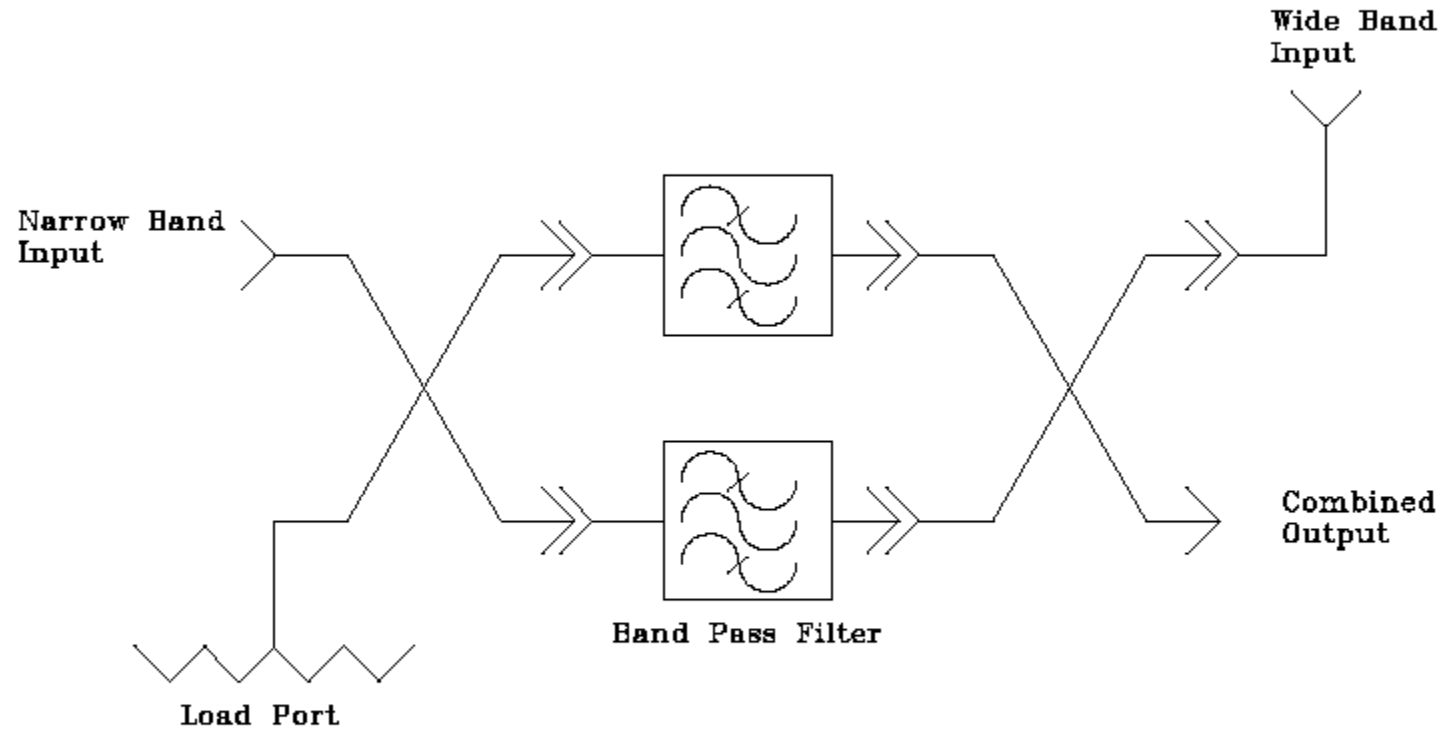
Constant Impedance (Balanced) Channel Combiners



CICC Narrowband Signal Flow

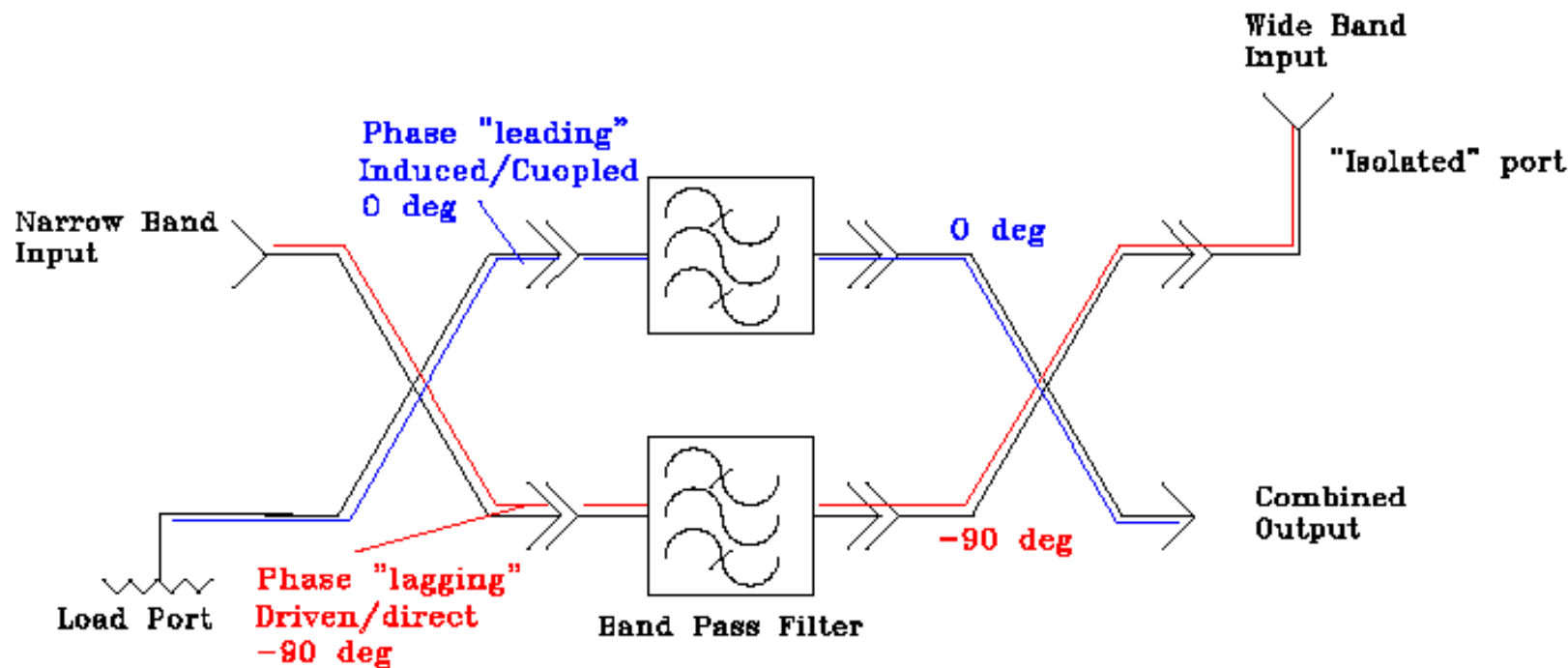

CICC Wideband Flow to Filters

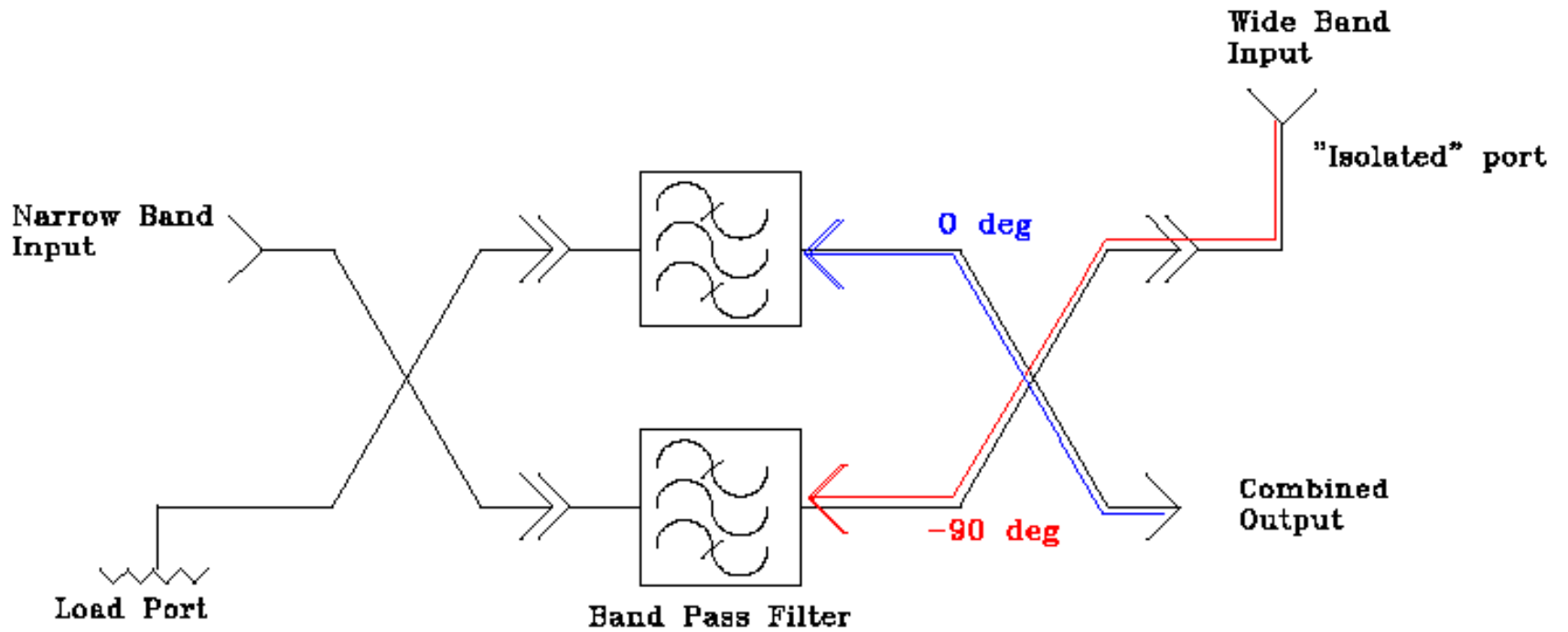

Constant Impedance (Balanced) Channel Combiners

- CICC's present wideband *matched* impedances at both the narrowband and wideband inputs.
- Each CICC module adds a single new channel to a pre-existing multiplex of channels.
- CICC's are modular and can be cascaded with other CICC modules.

The Role of the Hybrid in a Constant Impedance Channel Combiner


The Role of the Hybrid in a Constant Impedance Channel Combiner

- Splitting signals with a hybrid.
- Combining equal-power “half-signals” with a hybrid.
- The “short-circuit” VSWR of a hybrid as an estimator of combiner VSWR at the wideband input port.

Splitting Signals With a Hybrid

Input, 100%, 0°

Direct Output, 50%, -90°

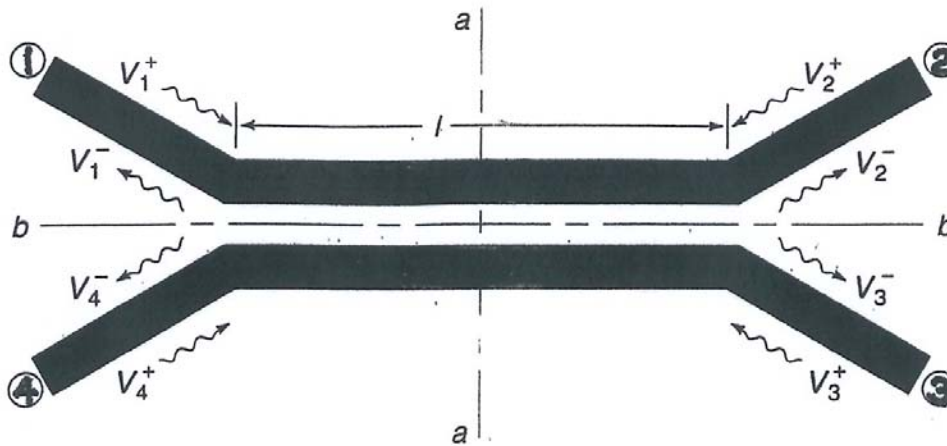

Coupled Output, 50%, 0°


Isolated Port



Combining Signals With a Hybrid

Isolated Port


Input 50%, -90°

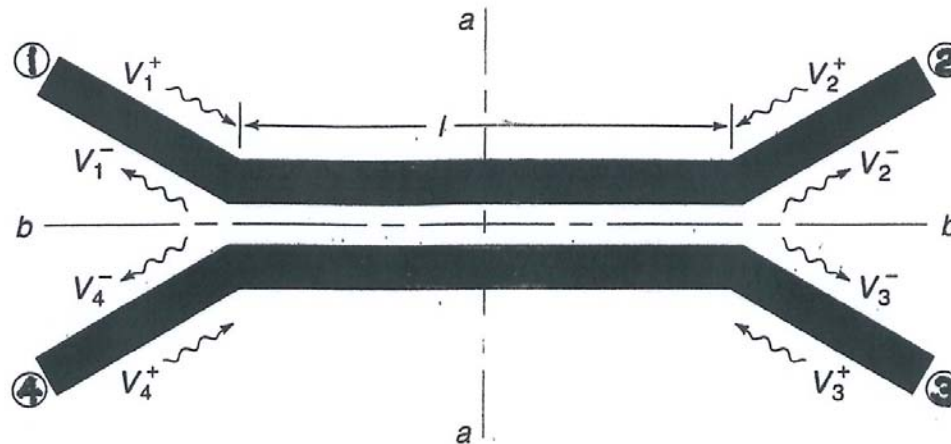

Input, 50%, 0°

Output 100%, -90°

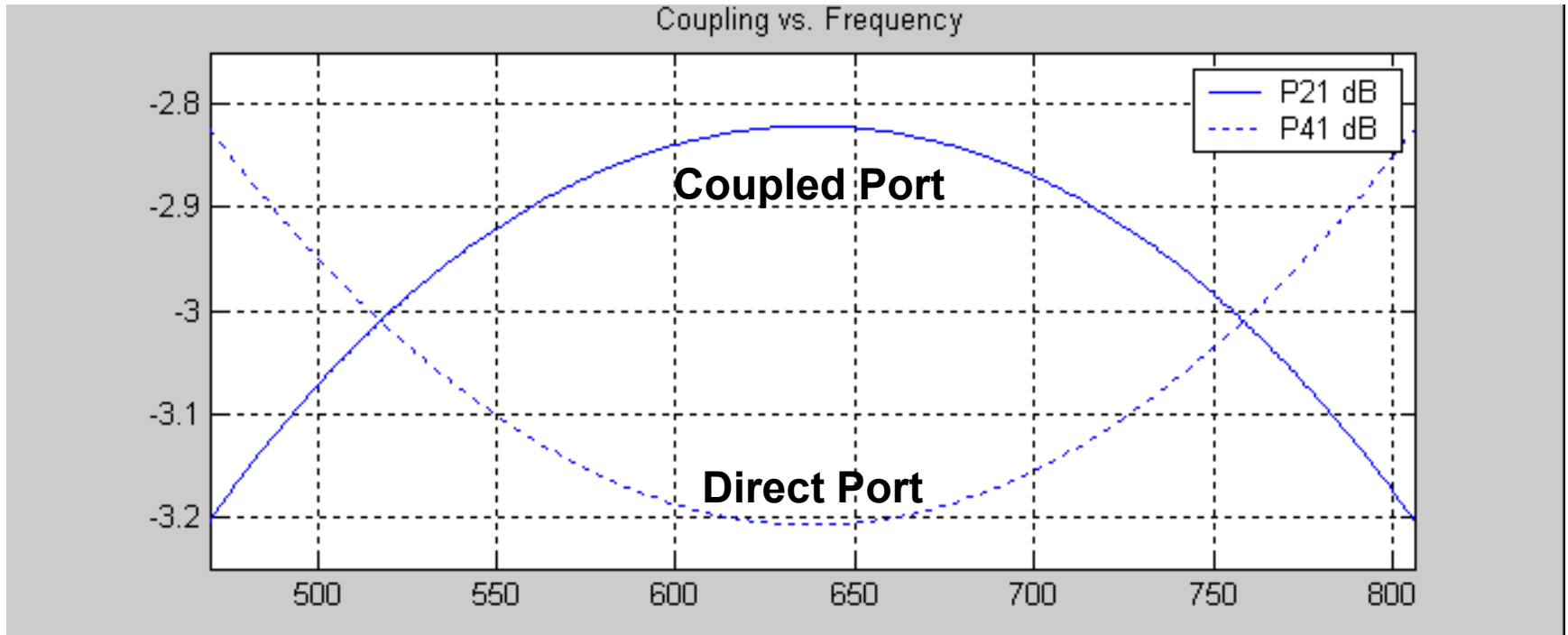Hybrid Amplitude Split and its Frequency Dependence




- **Broadband coupling of a quarter-wave hybrid**
- **The amplitude-imbalance is equalized across the band.**

Short Circuited, Over-coupled Hybrid

100% Input Power
Reflected 2.2%
16.5 dB RL
1.35 VSWR

47.8%, -90°, reflected back

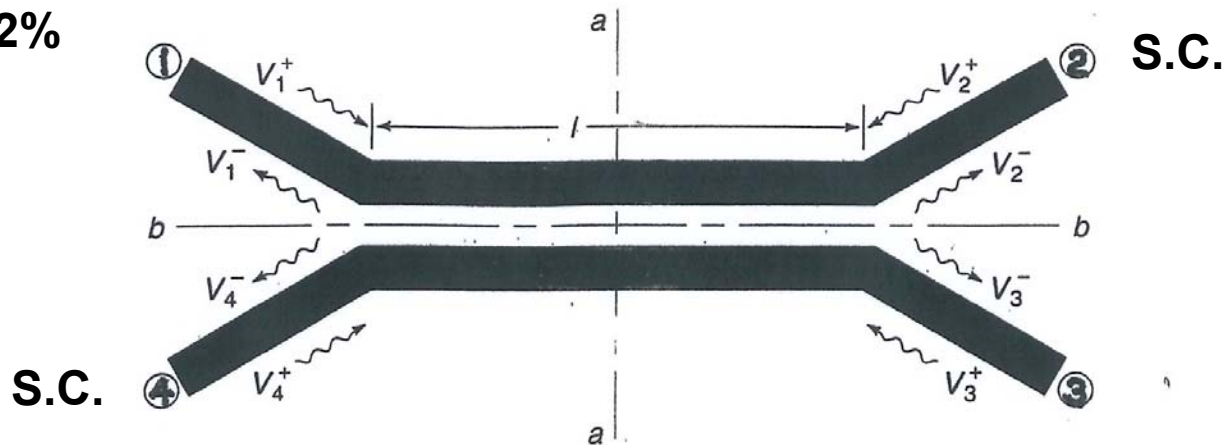

52.2%, 0°, reflected back

Output ?


“Short Circuit” VSWR

- Wideband signals entering a CICC are reflected by the filter and are recombined by the wideband hybrid.
- If the amplitude split of the hybrid is not a perfect -3.01 dB, then there will be some reflected power at the wideband input.
- This is essentially the same as the short-circuit VSWR of the hybrid, assuming filters are well matched.
- Thus, having a flatter amplitude split will lead to a CICC with better wideband input VSWR.

An Improved Hybrid

- The limitation of the quarter wave hybrid is its amplitude split versus frequency which is always the same cosine-squared shape.
- MCI has developed a multi-step hybrid that has flatter amplitude split and thus lower short-circuit VSWR

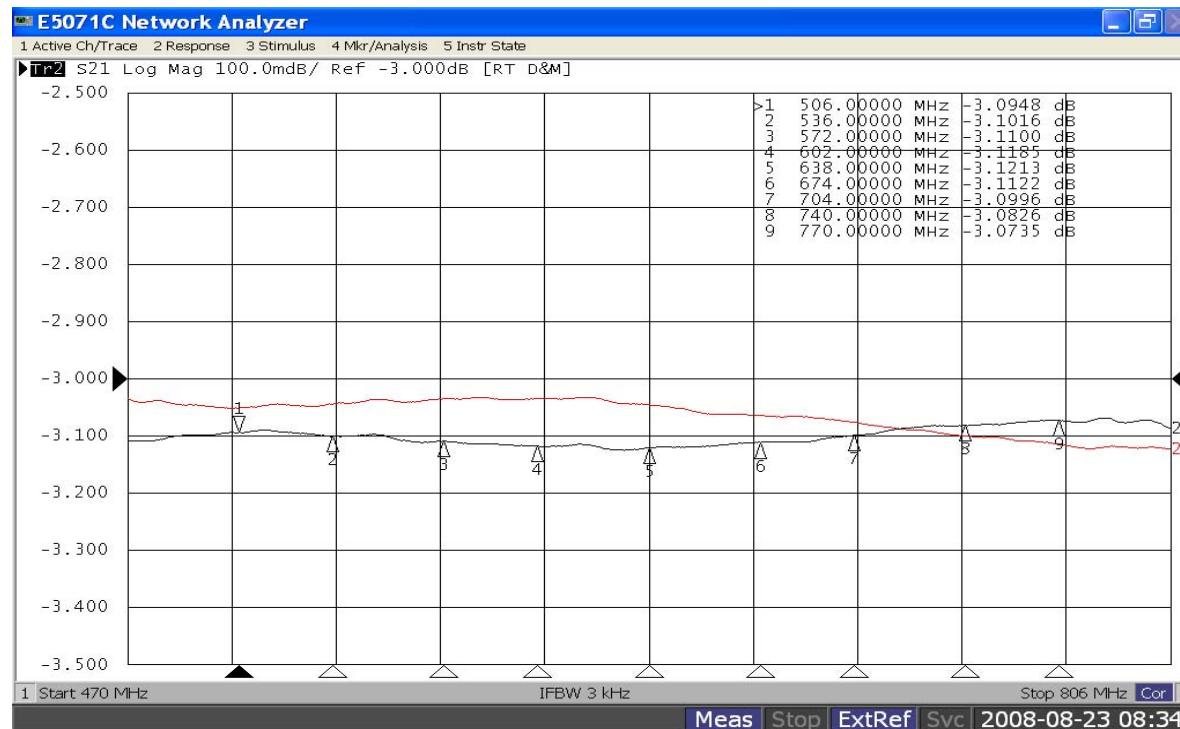Amplitude Split of Super-hybrid (multi steps) 470-806 MHz




- Only 0.08 dB maximum imbalance compared with 0.40 dB with a quarter-wave hybrid.
- This indicates 0.5% reflected power in short-circuit conditions, 23 dB RL,
- 1.15 VSWR as compared with 16.5 dB RL and 1.35 VSWR for standard hybrid.

E5071C Network Analyzer

1 Active Ch/Trace 2 Response 3 Stimulus 4 Mkr/Analysis 5 Instr State

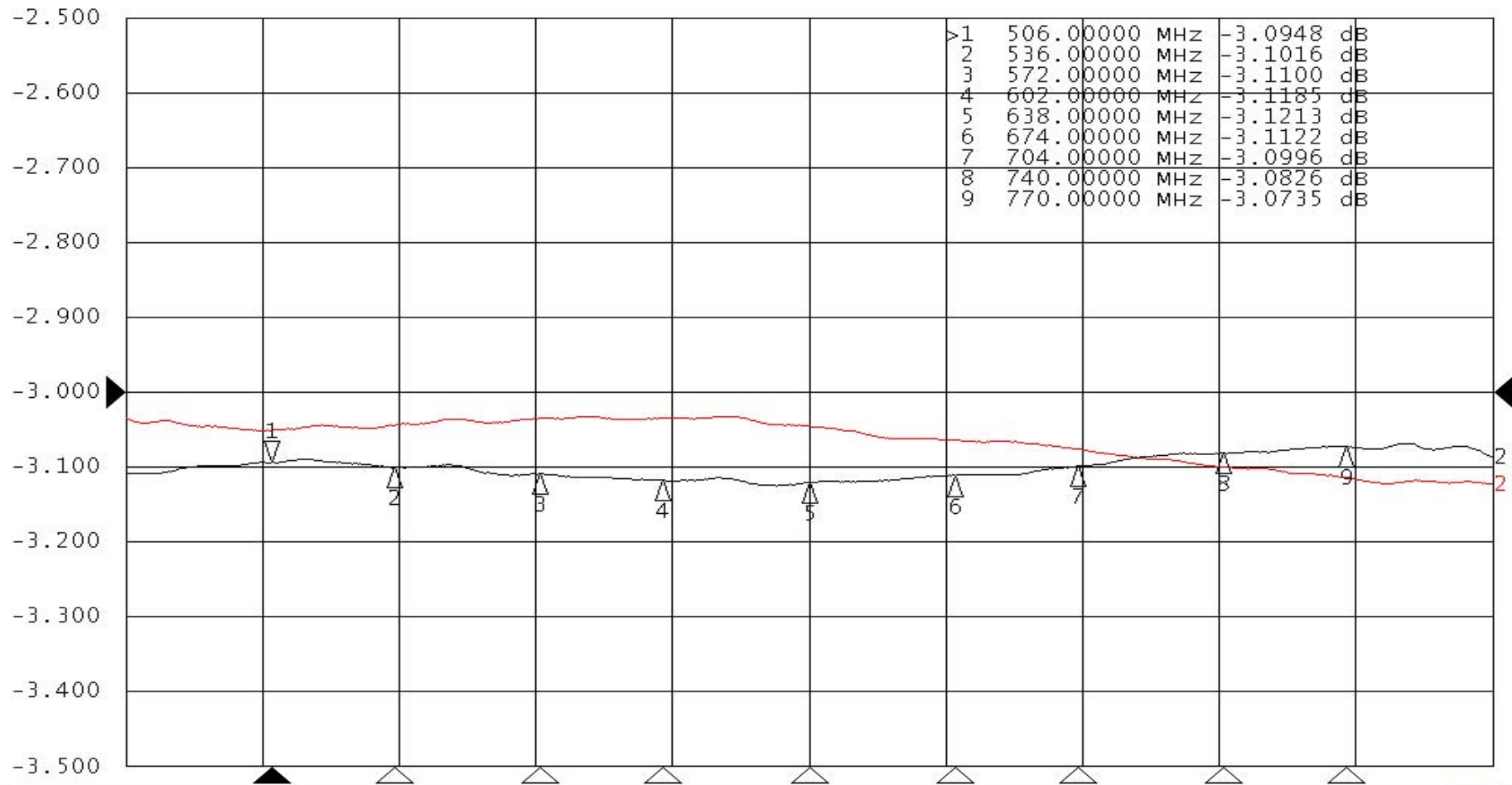Tr2 S21 Log Mag 100.0mdB/ Ref -3.000dB [RT D&M]




1 Start 470 MHz

IFBW 3 kHz


Stop 806 MHz Cor !

Meas Stop ExtRef Svc 2008-08-23 08:34

S.C. VSWR of Super-Hybrid

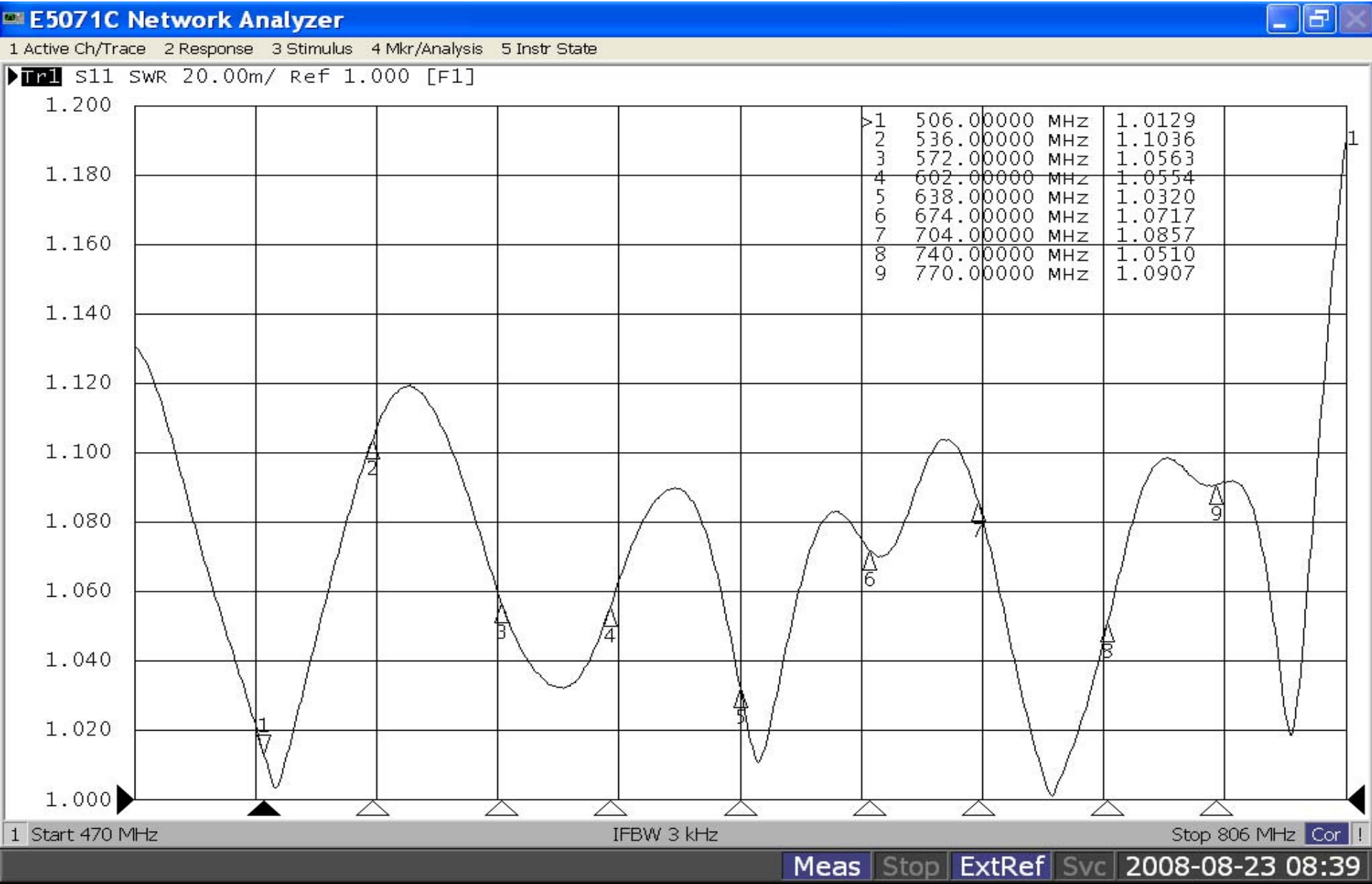

MCI new Superhybrid

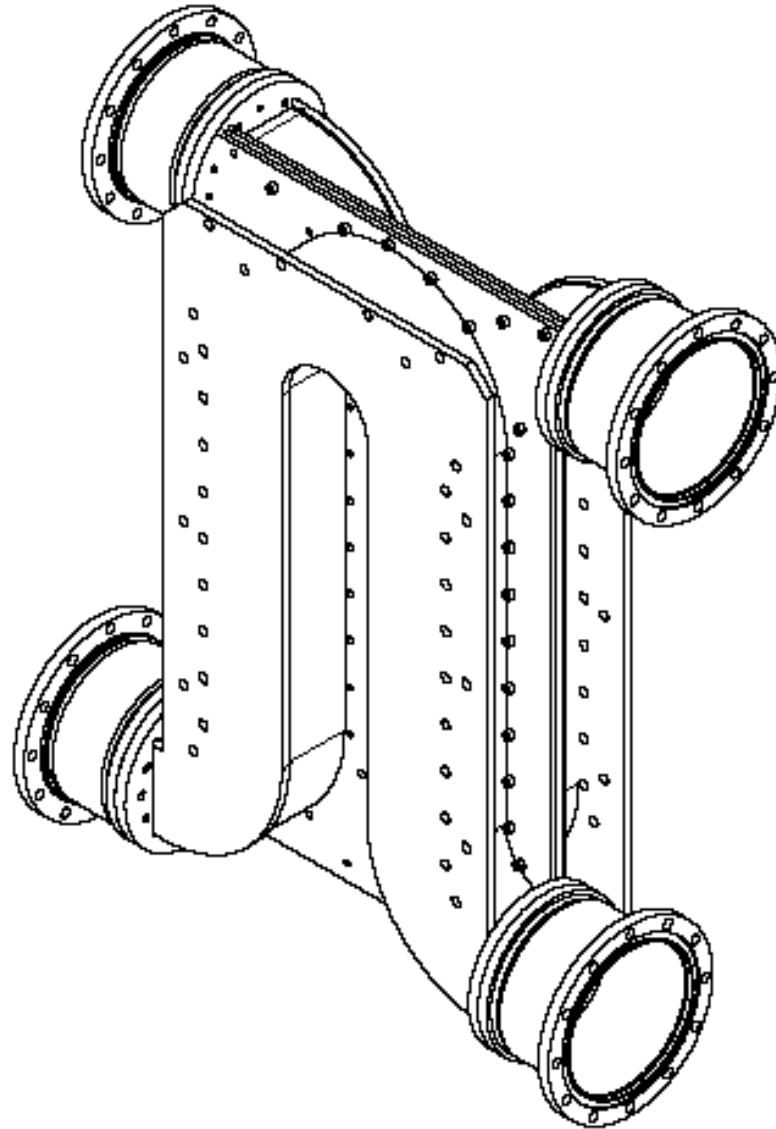



We have used our new Superhybrid with great results on three high power projects.

→ IonMedia Combiner, NB=ch22 at 48KW
WB = ch42, 54 & 55 at 15KW



→ VTC Combiner, NB=ch39 at 34KW
WB = ch33,34,38, 54, 60 & 61 at 65KW

→ Poland Combiner, NB= ch27&44 at 60KW
WB = ch33,41,48,51,55 &58 at 15KW


Ion Media CICC with Superhybrids

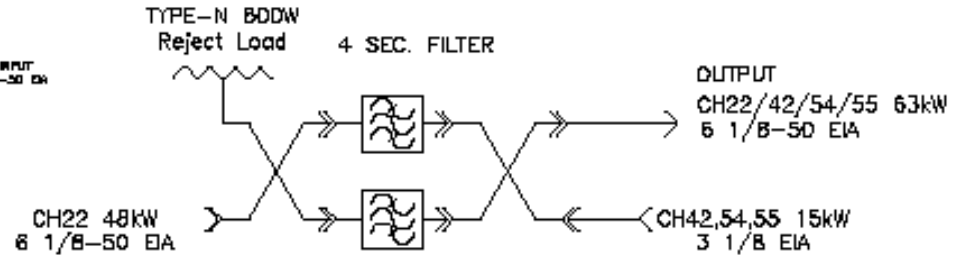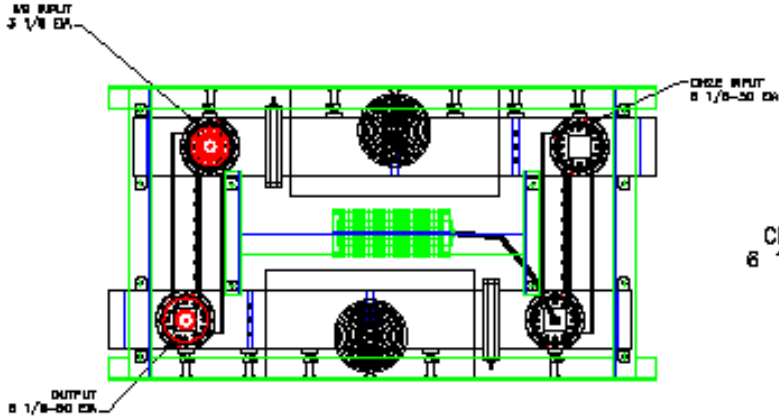

RF SCHEMATIC

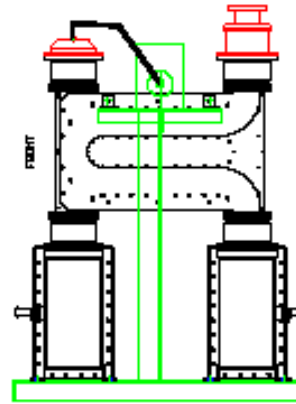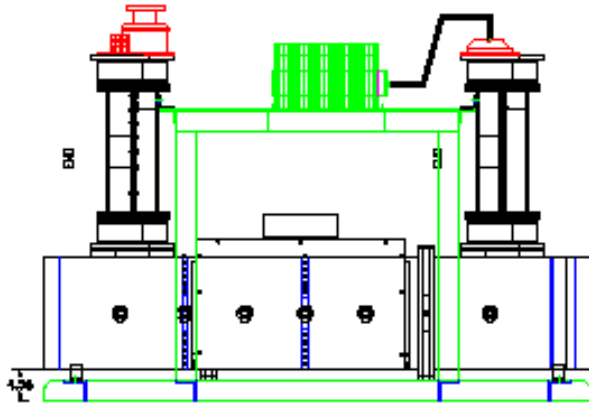



1 S11 SWR 20.00m/ Ref 1.000 [F1]

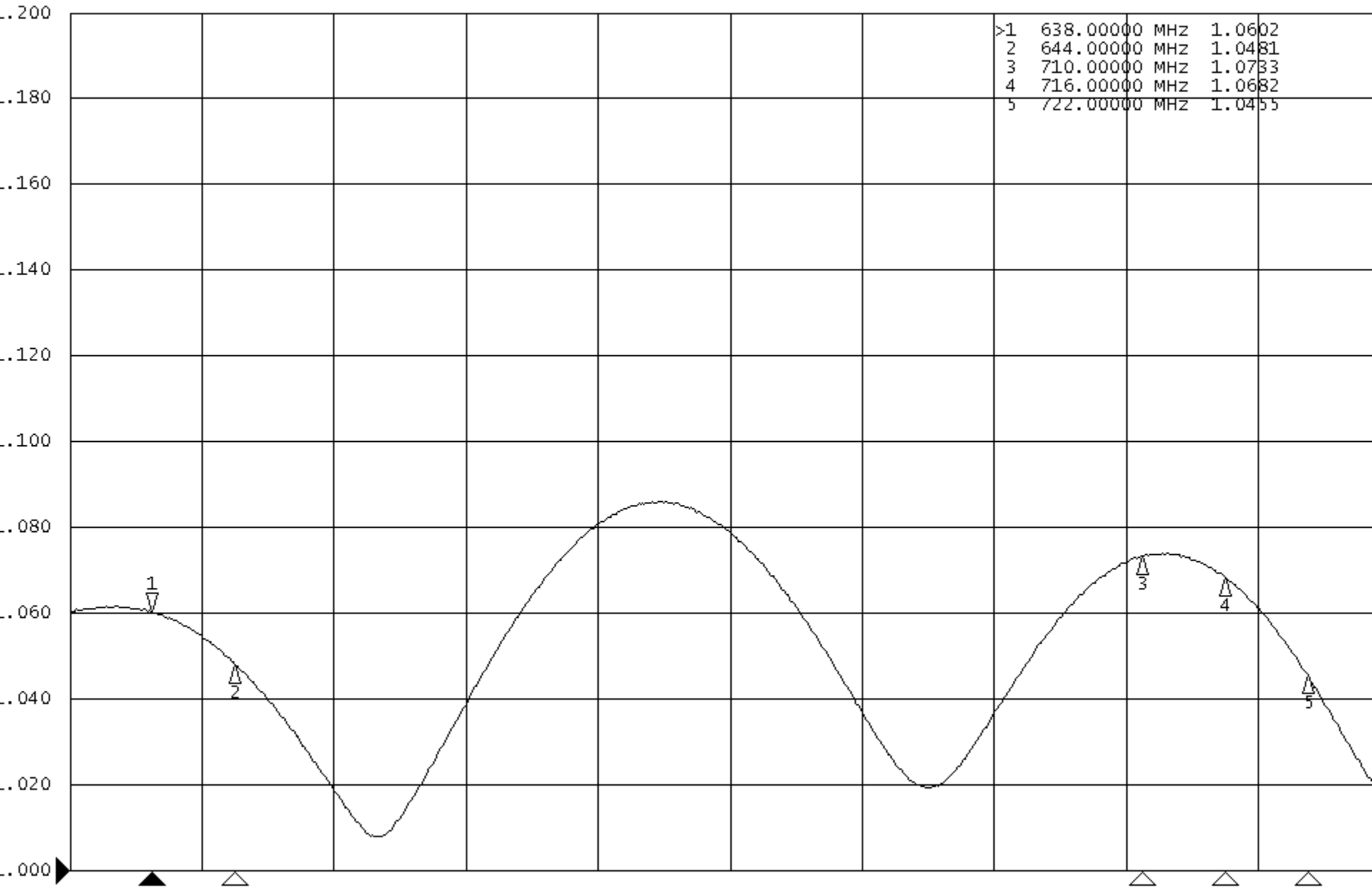


Can Tho Combiner 41276-8DMF-FB

6-1/8 CIBP-8DMF 2CH COMBINER




216133D-6325

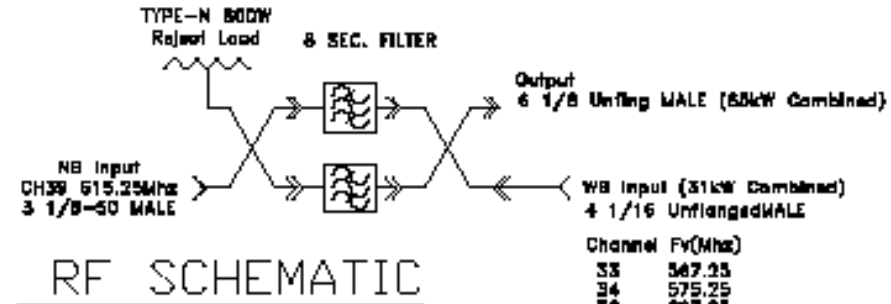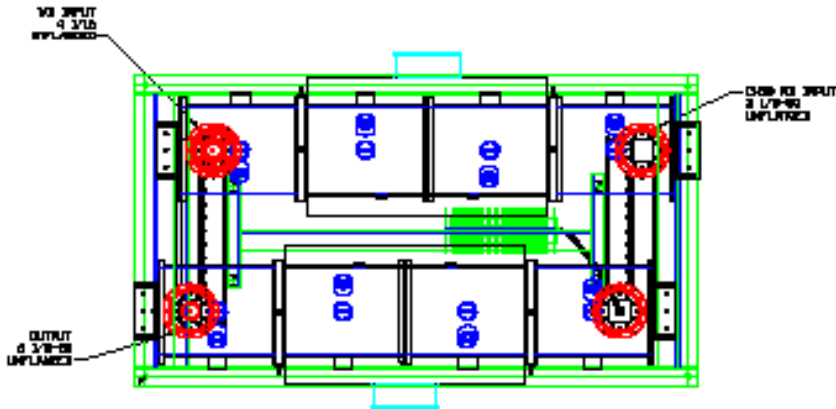

Channel	Fv(MHz)
33	567.25
34	575.25
38	607.25
54	735.25
60	783.25
61	791.25

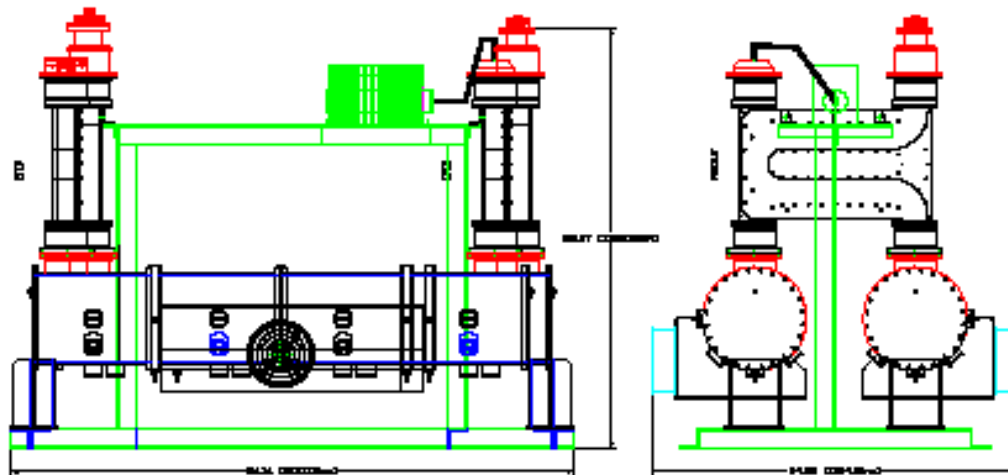

Poland Broadband Combiner

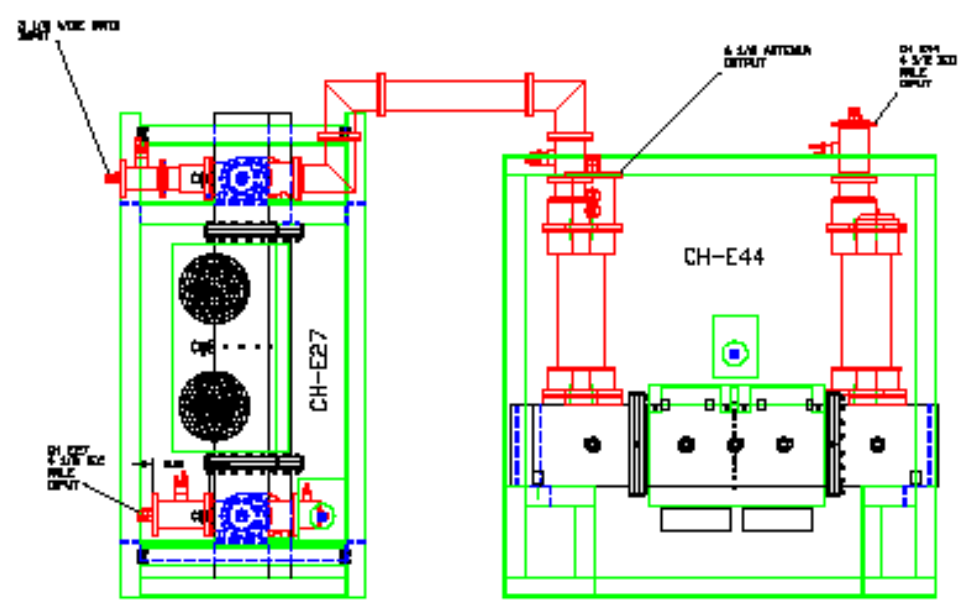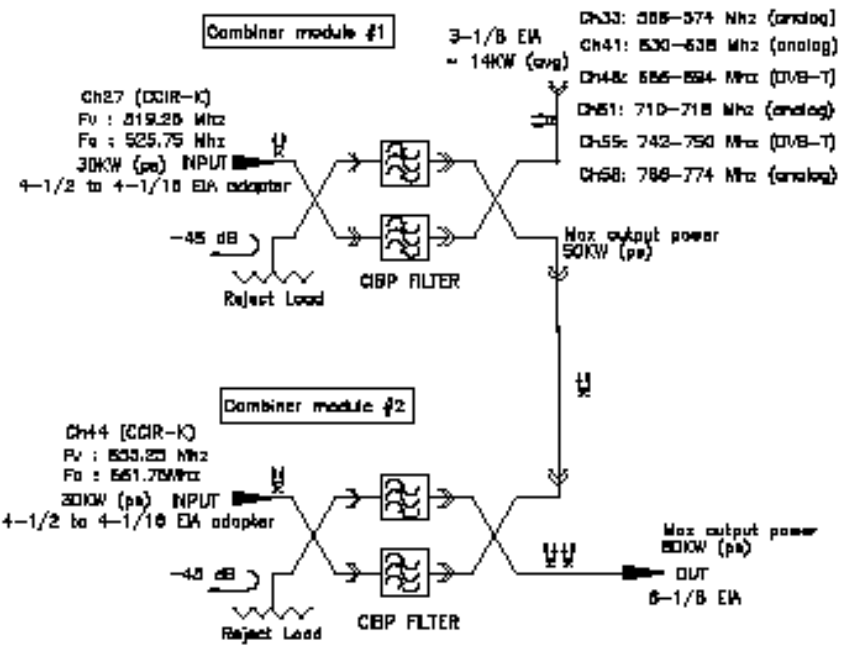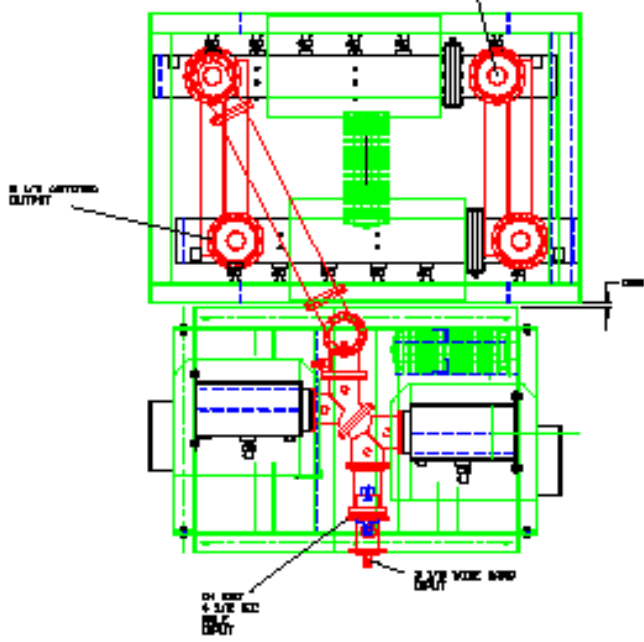


Thank you for your interest in Micro Communications



Please check out our website at www.mcibroadcast.com
for a complete copy of these presentations


Loop Combiners (Commensurate Line)

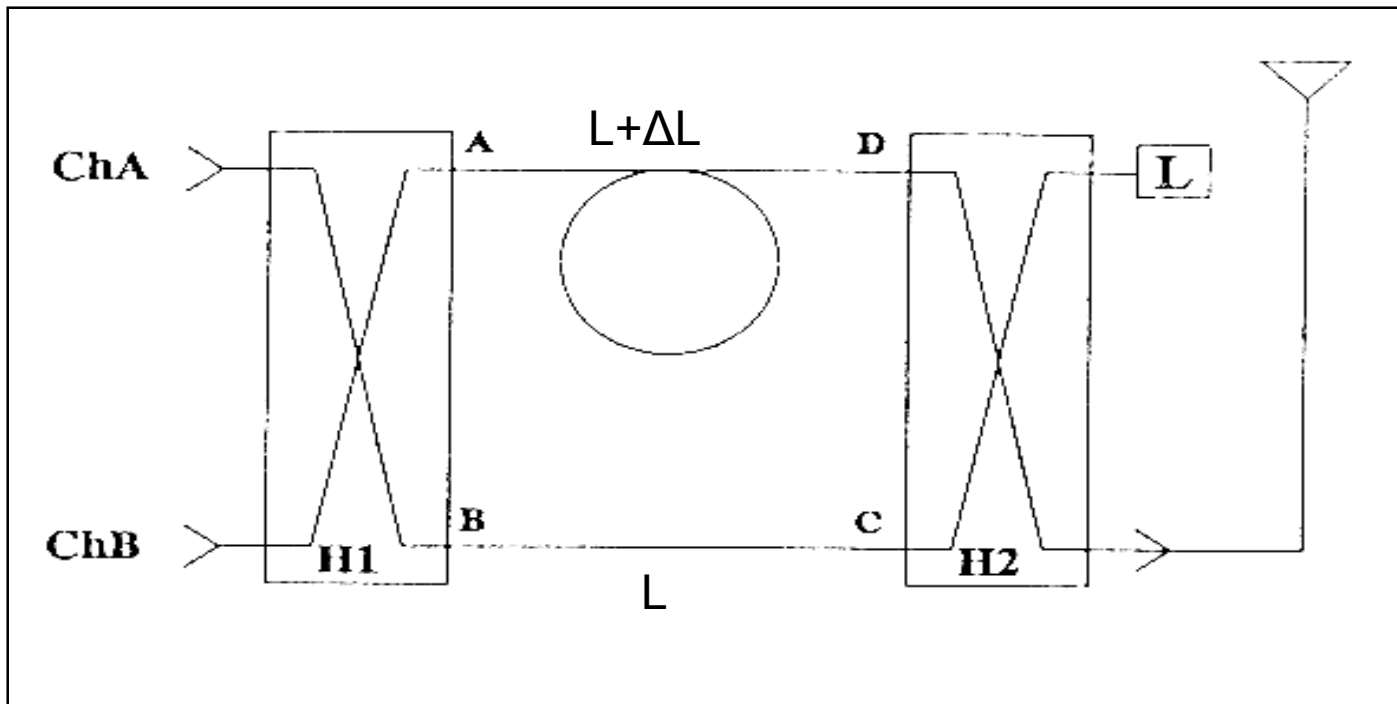

- Each channel is split by an input hybrid, phased by interconnecting cables and combined by an output hybrid.
- Proper phasing results in full transmission of both channels to the single output port.

Loop Combiners


Channel A Solutions

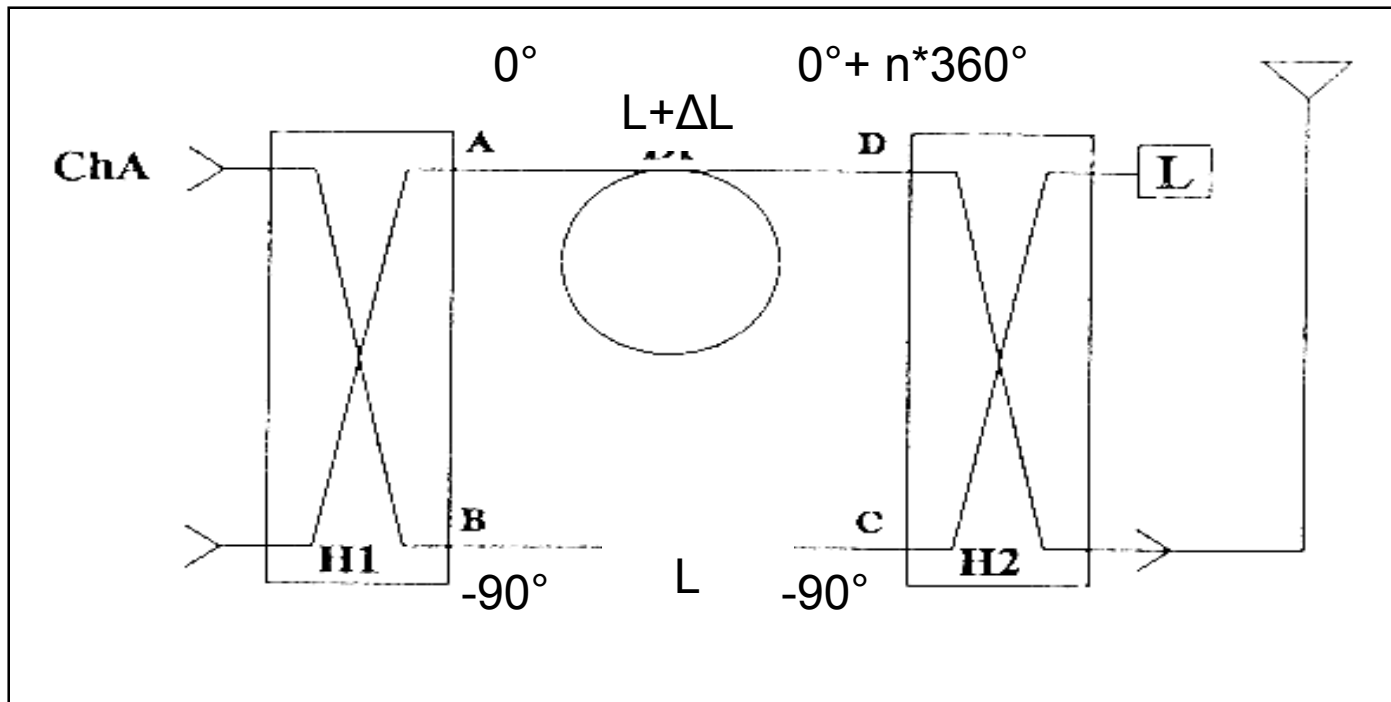

- The required differential line length for Channel A is any integer multiple of wavelength λ_A ,
$$\Delta L = n\lambda_A, \text{ where } n \text{ is any integer}$$
- This results in no change to the relative phase.

Loop Combiners

Channel B Solutions

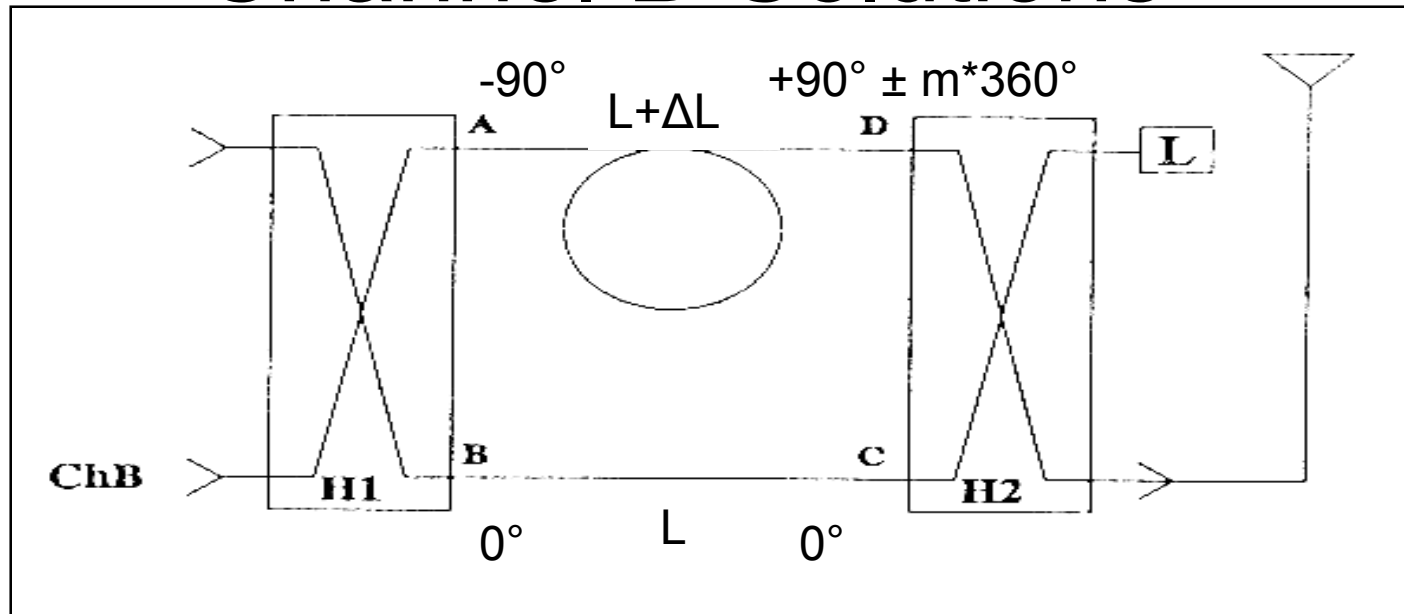


- The required differential line length for Channel B is any *odd* half-wavelength, e.g. $\lambda_B/2$, $3\lambda_B/2$, $5\lambda_B/2$, ...

$$\Delta L = (2m-1)*\lambda_B/2, \text{ where } m \text{ is any integer}$$

- This inverts the relative phase, changing it by 180°.
- We can subtract 90° from the top and bottom values without changing the relative phase, resulting in

Loop Combiners

Channel B Solutions

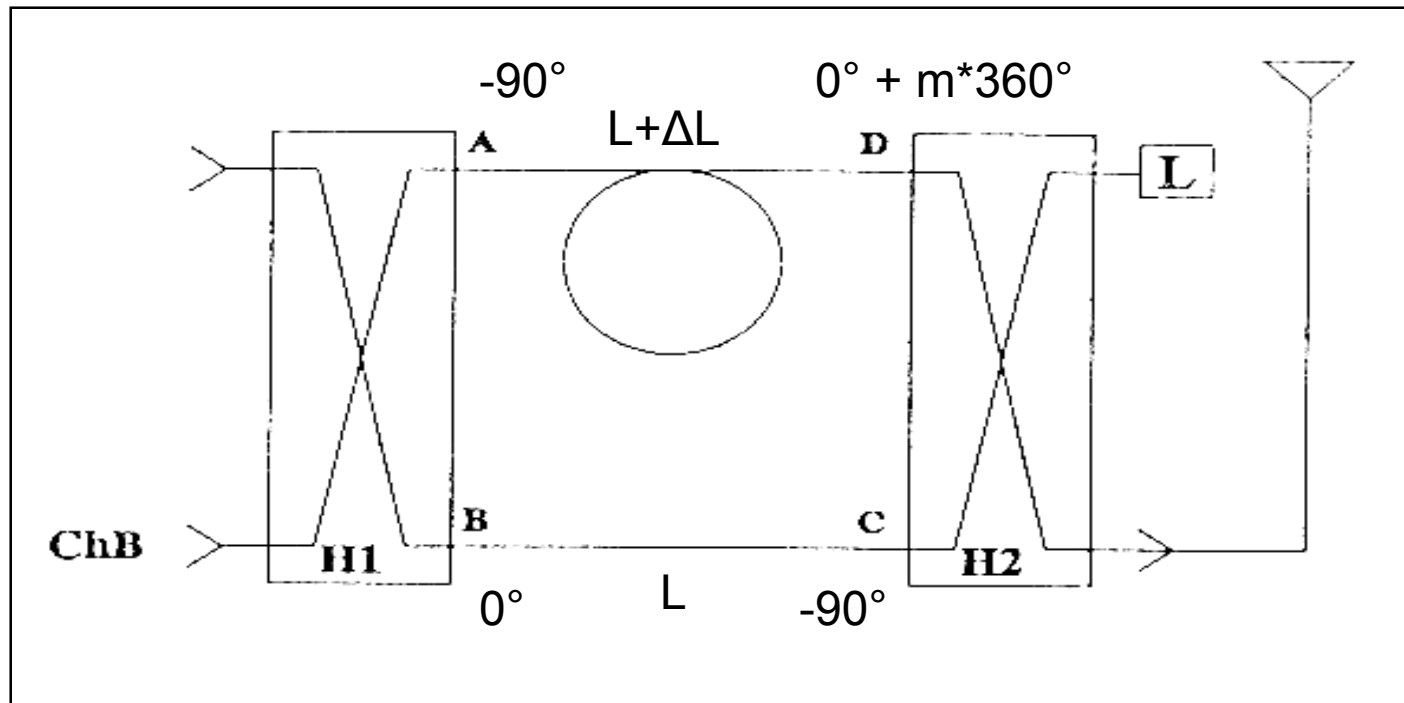

- Notice that the phase-lagging leg (upper) becomes the phase-leading leg and vice versa.
- This phases the half-signals for recombination to the antenna port



Loop Combiners

Two-Channel Solution

Two conditions govern the differential line length ΔL

$$\Delta L = n\lambda_A, \text{ where } n = 1, 2, 3, \dots$$

$$\Delta L = (2m-1)\lambda_B/2, \text{ where } m = 1, 2, 3, \dots$$

Combining these two equations we get the required relationship between integers n and m .

$$(2m-1)\lambda_B/2 = n\lambda_A$$

By dividing both sides by λ_B we get

$$m-1/2 = n (\lambda_A/\lambda_B)$$

This problem has no closed-form solution. It is solved graphically, or by computer search.

Loop Combiners

- Require no filters.
 - No group delay variations
 - Low loss, potentially very high power
- Provides no filtering.
- Very rugged and hard to detune.
- Simple to design and build.
- Limited to two, well-separated channels
- Typically more expensive than Starpoint combiners.

Loop Combiner

